




Technologies Pvt Ltd

<b>SYNCHRONOUS CIRCUITS</b>	<b>ASYNCHRONOUS CIRCUITS</b>
1) These are the sequential circuits which are governed by a global clock signal.	1) These are circuits which are governed by a input signals regardless of clock signal.
2) The state of all elements of a synchronous circuit changes only by an application of a distributed clock signal.	2) Asynchronous circuits change state through the inputs received by them.
<b>Pros:</b> 1) The state of a synchronous circuit predictable.	<b>Cons:</b> 1) The state of asynchronous circuits are unpredictable.
2) synchronous clock signals are less susceptible to noise, there is no chance for race conditions.	2) asynchronous circuits can transition into a wrong state due to incorrect arrival time of 2 inputs, race condition will occur.
3) clock impulses are given are same for all the flip flops so it is very easy to design any circuit.	3) More complex to design

<p>4) Easy to trouble shoot since predictable</p>	<p>4) Not easy to troubleshoot</p>
<p>5) Circuit is more reliable and portable.</p>	<p>5) Circuit is not reliable</p>
<p><b>Cons:</b> 1) The time period of a clock signal should be long enough to accommodate longest propagation delay</p>	<p><b>Pros:</b> 1) They are limited by propagation delay of logic gates only.</p>
<p>2) Practically all the circuits today are synchronous circuits, except the part where speed of the circuit operation is crucial.</p>	<p>2) These are used primarily in high speed systems such as Signal Processing hardware.</p>

Example:

 


## Synchronous D flip flop

lop is only operated with respect to clock so its output will change with respect clock.

### Verilog code:

```
module dflip_flop(d,q,clk,reset);  
input d,clk,reset;  
output reg q;  
always@(posedge clk)  
begin  
if (!reset)  
    q<=0;  
else
```

```
q<=d;  
end  
endmodule
```

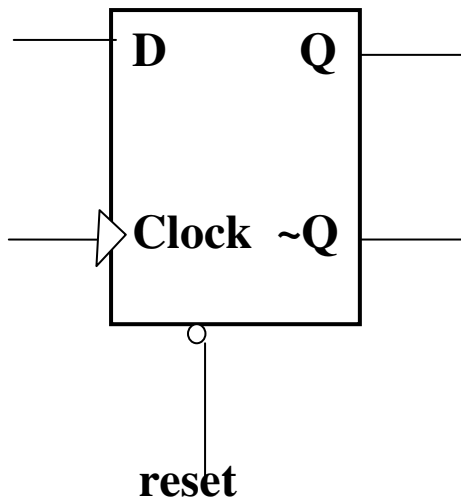

Asynchronous D flip  
flop



In above diagram the d flip flop is operated with respect to both clock and reset condition so the output will change whenever the reset condition changes it will not wait for clock to change

**Verilog code:**

```
module dfli_flop(d,q,clk,reset);  
input d,clk,reset;  
output reg q;  
always@(posedge clk or negedge reset)  
begin  
if (!reset)  
    q<=0;  
else  
    q<=d;  
end  
endmodule
```